
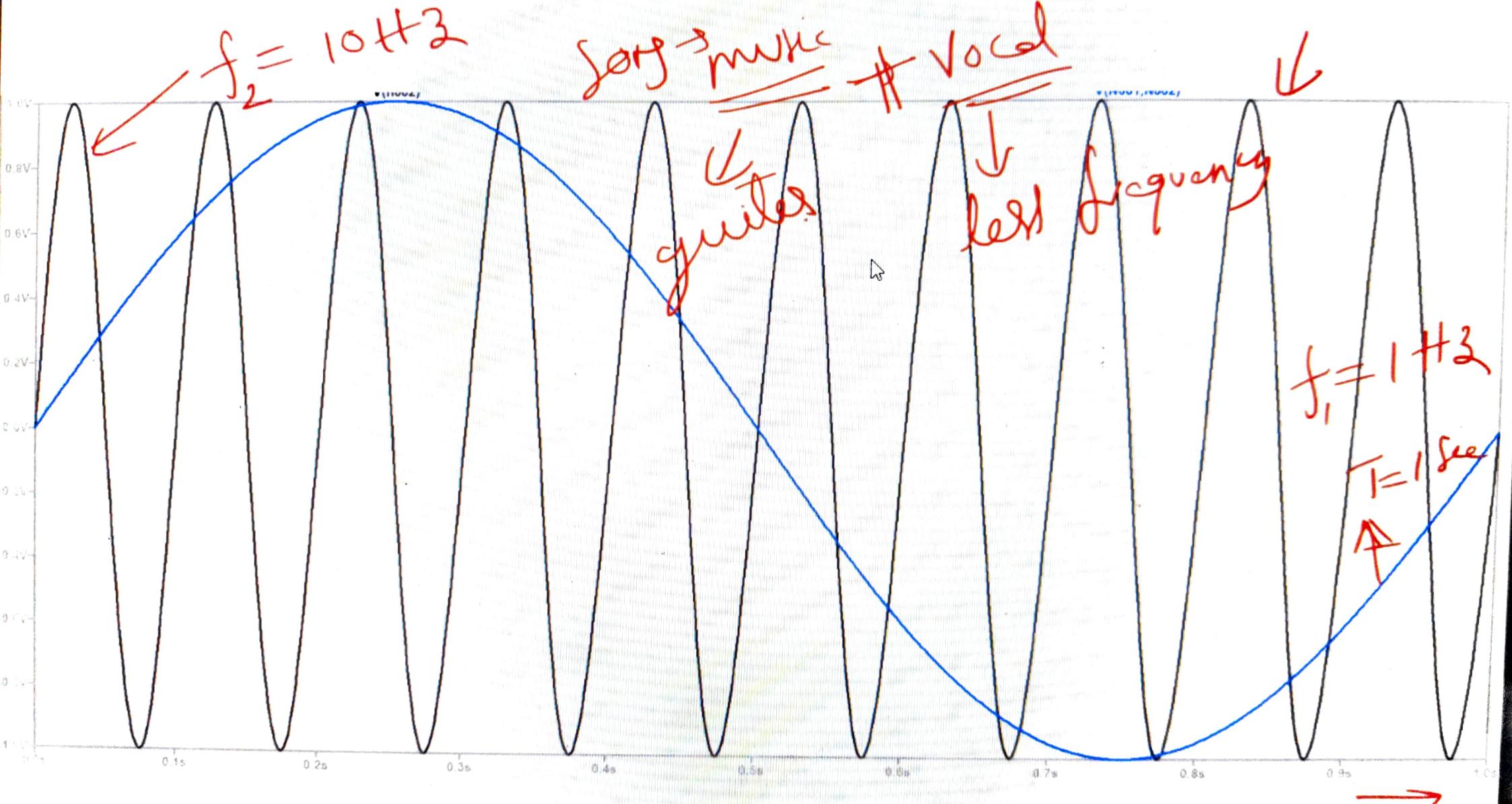


Active Filters

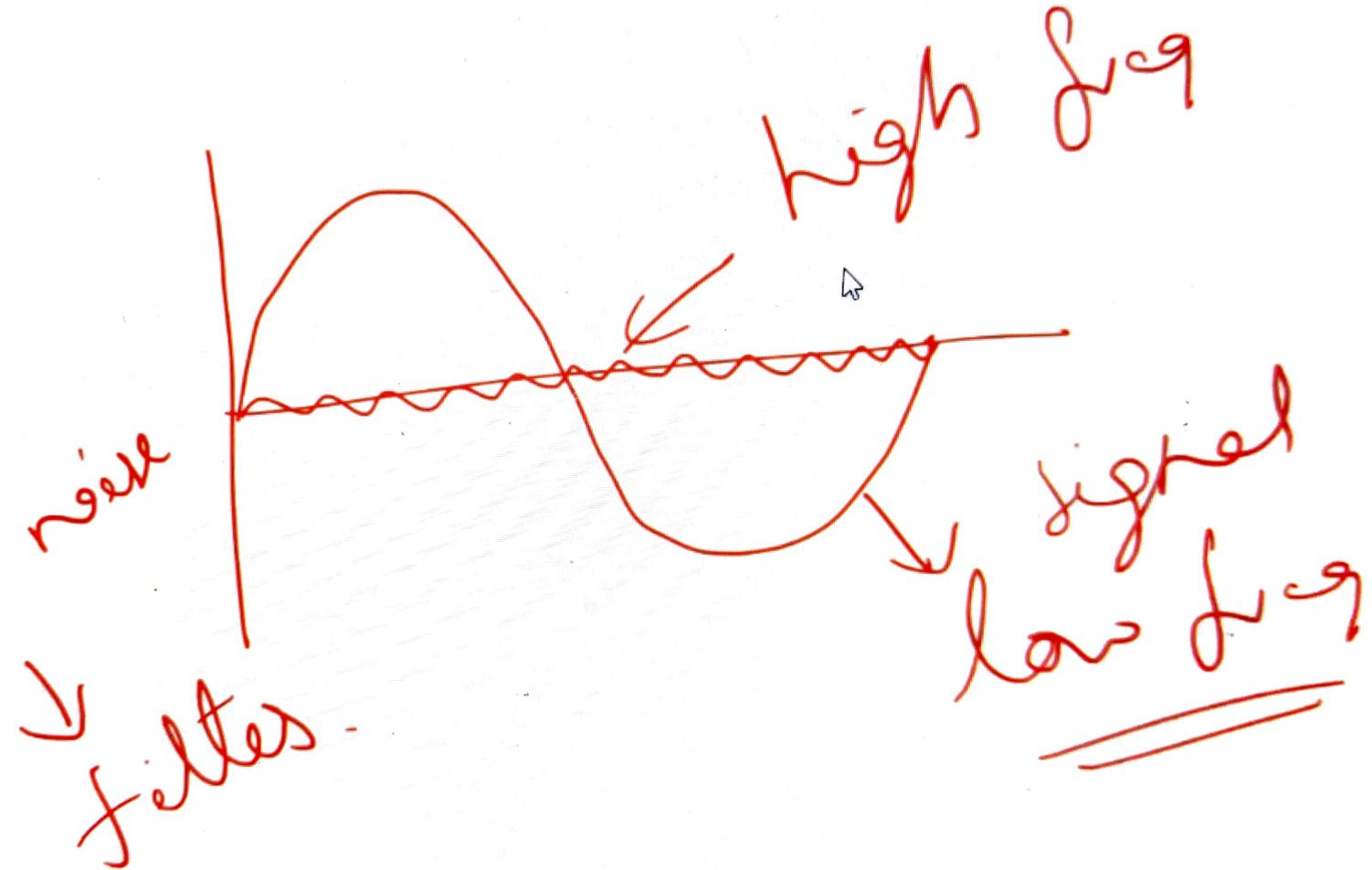



Self-gated
signal from
from filters



Electric filters





Filter: Which allows/pass the input signals to the output in desired range of frequencies

- Passive filters (R, L, C)
 - Input signal is not amplified
- Active filters (transistors, op-amps)
 - Input signal is amplified

Filter classification

- Low pass filter (LPF)
- High pass filter (HPF)
- Band pass filter (BPF)
- Band reject filter/Band stop filter (BSF)

Frequency response of various filters

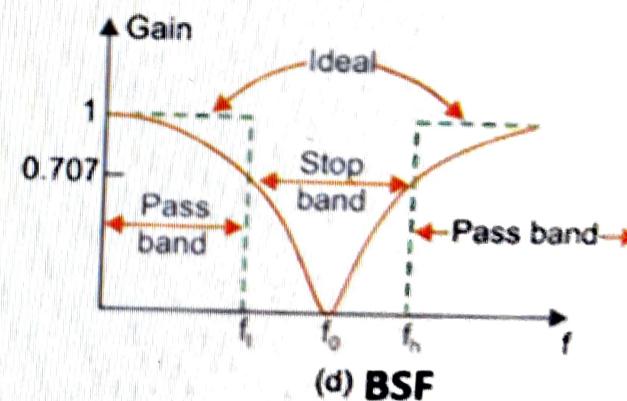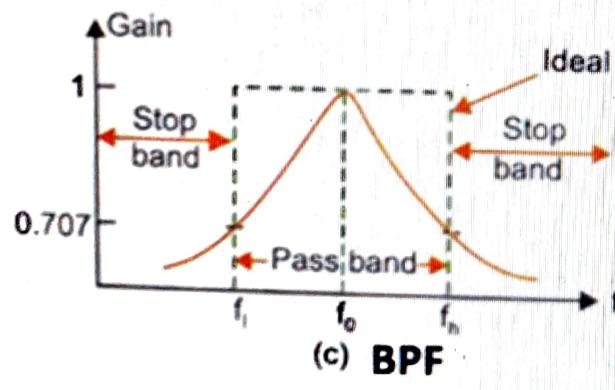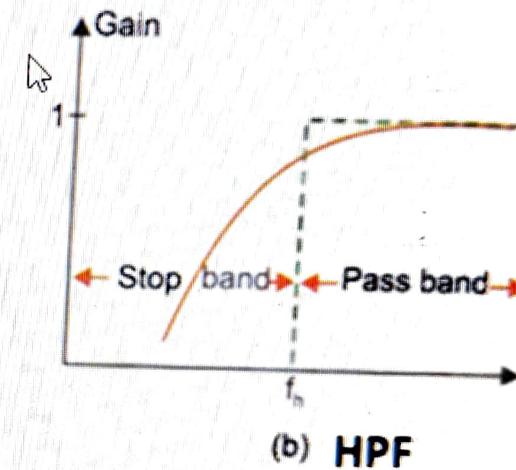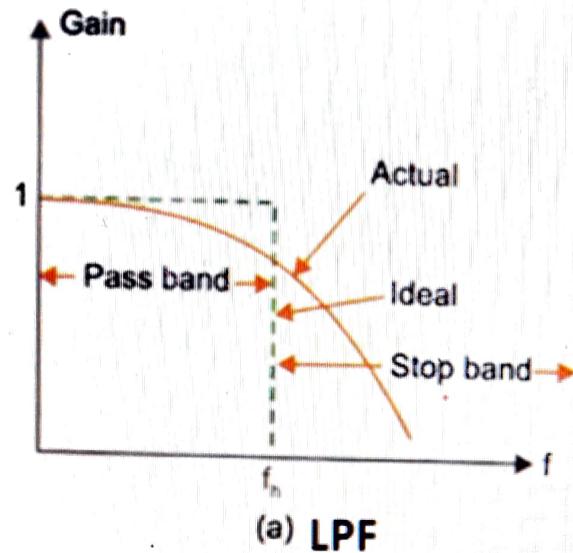

Passive Low-Pass RL filter




- Transfer function of RL LPF

$$V_o = \frac{R}{R + j\omega L} V_i \rightarrow H(j\omega) = \frac{V_o}{V_i} = \frac{R}{R + j\omega L} = \frac{1}{1 + j(\omega L/R)}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega L/R)^2}}$$

Cut-off frequency

- Ideal filter: The frequency between the pass- and-stop bands is called the cut-off frequency (ω_c)
- Practical filter: The frequency at which the magnitude $|H(j\omega)|$ is reduced to $1/\sqrt{2}$ ($=0.7$) times the maximum magnitude

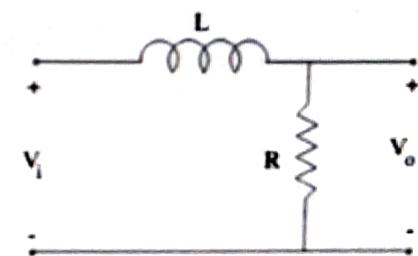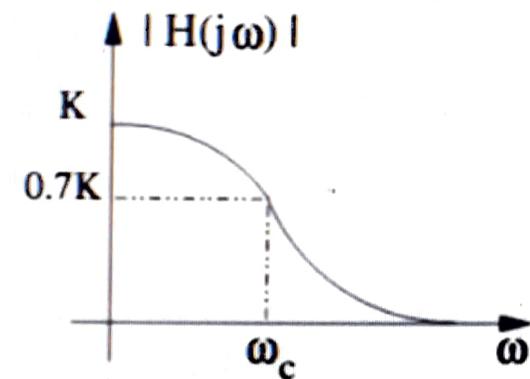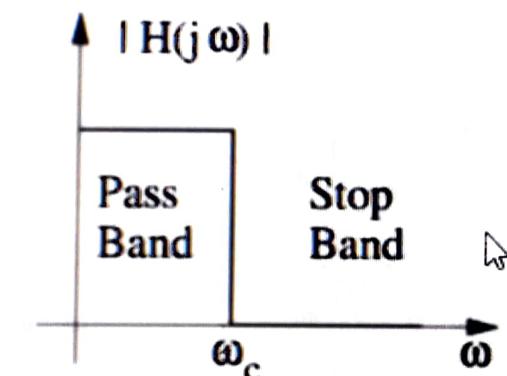

Passive Low-Pass RL filter




AC
R L C
Impedance - Z
 $Z = R + jX_L + jX_C$
 $= R + j(X_L - X_C)$
 $X_L \rightarrow$ Inductive

$$V_o = \frac{R}{R + j\omega L} V_i \rightarrow H(j\omega) = \frac{V_o}{V_i} = \frac{R}{R + j\omega L} = \frac{1}{1 + j(\omega L/R)}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega L/R)^2}}$$

Cut-off frequency

- Ideal filter: The frequency between the pass- and-stop bands is called the cut-off frequency (ω_c)
- Practical filter: The frequency at which the magnitude $|H(j\omega)|$ is reduced to $1/\sqrt{2}$ ($=0.7$) times the maximum magnitude

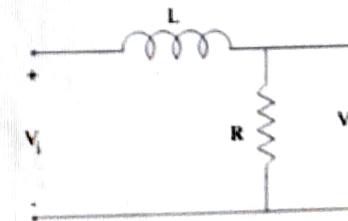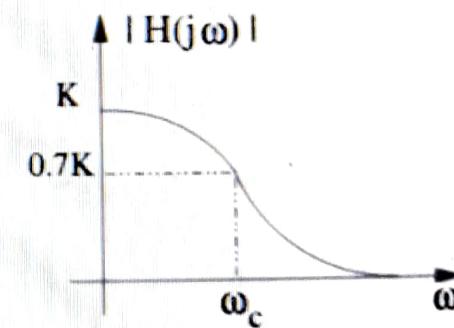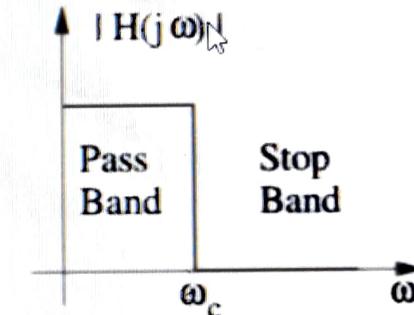


DC ckt
Resistance

RC

$$z = R + j(X_L - X_C)$$

↑
real ↑
 imaginary part

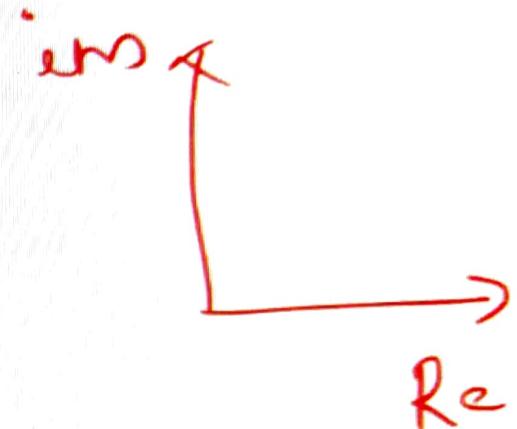

$$\left. \begin{aligned} |z| &= \sqrt{R^2 + (X_L - X_C)^2} && \text{RL C/L} \\ \theta &= \tan^{-1}\left(\frac{X_L - X_C}{R}\right) && z = R + jX_L \end{aligned} \right/ |z| = \sqrt{R^2 + X_L^2}$$

$$\left. \begin{aligned} & R \subset \\ |z| &= \sqrt{R^2 + X_C^2} \end{aligned} \right/$$


$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}}$$

at $f=0 H3$

$$\rightarrow |H(j0)| = \frac{1}{0} = \infty$$

$f=\infty H3$

$$\rightarrow |H(j\infty)| = \frac{1}{\infty} = 0$$

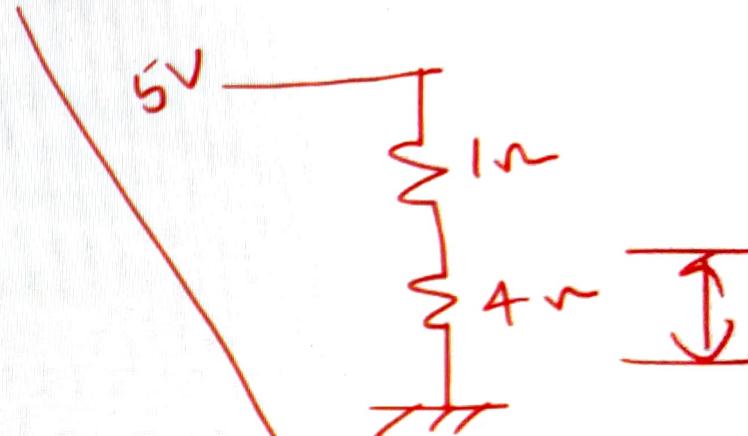

$$\frac{4}{1+4} \times 5 = \underline{\underline{4V}}$$

Cut-off frequency of RL LPF

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}}$$


At $f = 0 \text{ Hz}$,

$$|H(j\omega)| = 1$$

At $\omega = \omega_c$, $|H(j\omega)| = 1/\sqrt{2}$

$$\frac{1}{\sqrt{1 + \left(\frac{\omega_c L}{R}\right)^2}} = \frac{1}{\sqrt{2}}$$
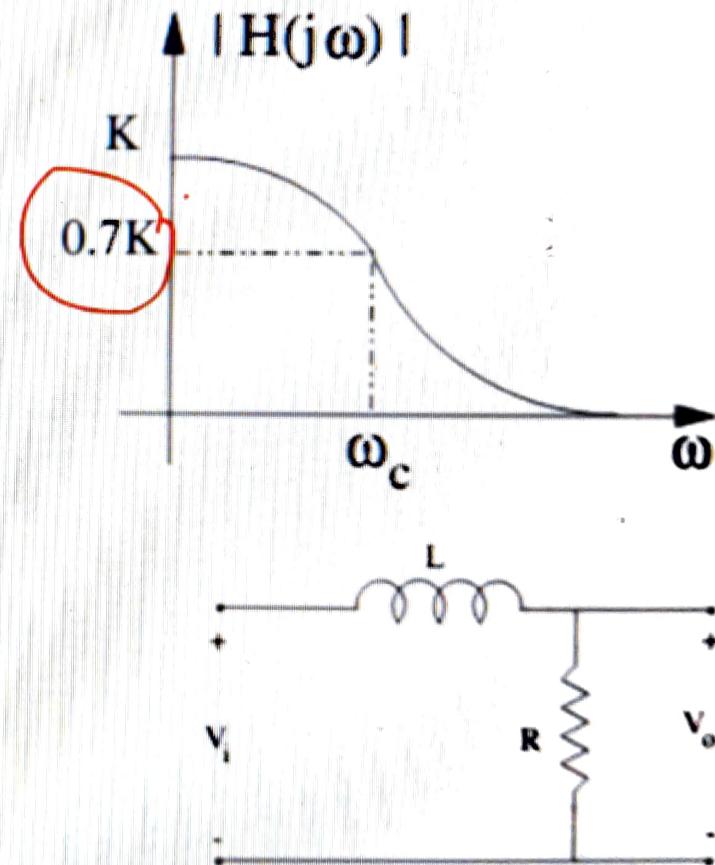
$$\omega_c = \frac{R}{L} \text{ and } H(j\omega) = \frac{1}{1 + j\left(\frac{\omega}{\omega_c}\right)}$$



Cut-off frequency of RL LPF

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}}$$


At $f = 0 \text{ Hz}$,

$$|H(j\omega)| = 1$$

At $\omega = \omega_c$, $|H(j\omega)| = 1/\sqrt{2}$

$$\frac{1}{\sqrt{1 + \left(\frac{\omega_c L}{R}\right)^2}} = \frac{1}{\sqrt{2}} = 0.7$$
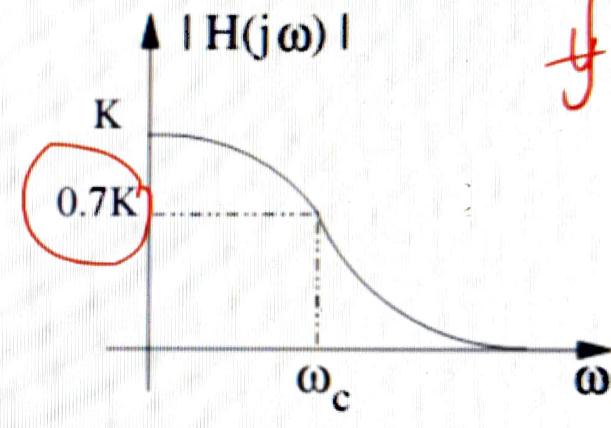
$$\omega_c = \frac{R}{L} \text{ and } H(j\omega) = \frac{1}{1 + j\left(\frac{\omega}{\omega_c}\right)}$$



2 KHz

$$f_c = \underline{\underline{1 \text{ KHz}}}$$

$$1 + \left(\frac{\omega_c L}{R}\right)^2 = 2$$


$$\frac{\omega_c L}{R} = 1$$

$$\omega_c = \frac{R}{L} \Rightarrow \left(f_c = \frac{R}{2\pi L}\right)$$

RC Low Pass Filter Circuit

$$V_o = \frac{1/(j\omega C)}{R + 1/(j\omega C)} V_i = \frac{1}{1 + j(\omega RC)} V_i$$
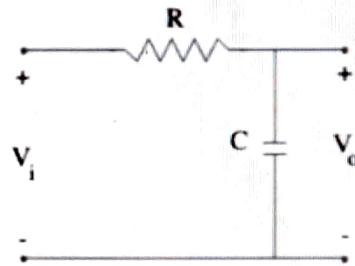
$$H(j\omega) = \frac{1}{1 + j\omega RC}$$



$$V_o = \frac{Z_C}{Z} V_i$$

$$Z_C = -jX_C = -j/\omega C$$

$$|H| = \frac{1}{\sqrt{1 + (\omega RC)^2}} = \frac{1}{j\omega C}$$

$$\theta_o = \left. \angle H \right| = -90^\circ$$

$$= \frac{Z_C}{R - jX_C} = \frac{-jX_C}{R - jX_C}$$

$$j^2 = -1$$

$$j = -\frac{1}{j}$$

Low Pass Filter Example


A Low Pass Filter circuit consisting of a resistor of $4.7 \text{ k}\Omega$ in series with a capacitor of 47 nF is connected across a 10 V sinusoidal supply. Calculate the output voltage (V_{out}) at a frequency of 100 Hz , 200 Hz and again at frequency of 10kHz , 11 kHz .

$$X_c = \frac{1}{2\pi fC}$$

$$Z = R - jX_c$$

$$|Z| = \sqrt{R^2 + X_c^2}$$
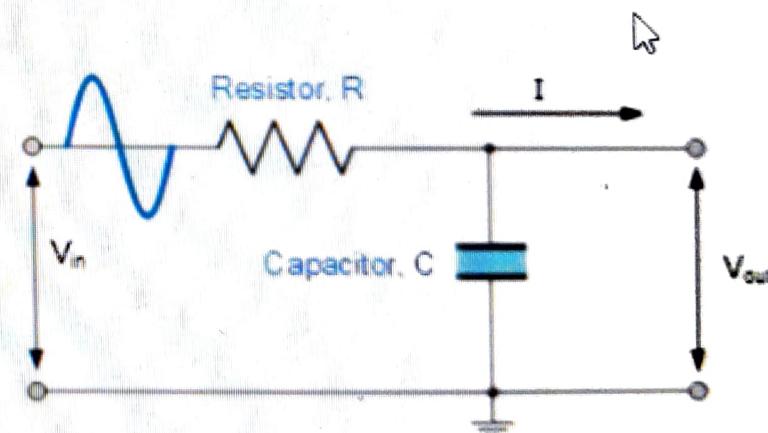
$$V_{out} = V_{in} \frac{X_c}{\sqrt{R^2 + X_c^2}} = V_{in} \frac{X_c}{Z}$$



Low Pass Filter Example


A Low Pass Filter circuit consisting of a resistor of $4.7 \text{ k}\Omega$ in series with a capacitor of 47 nF is connected across a 10 V sinusoidal supply. Calculate the output voltage (V_{out}) at a frequency of 100 Hz , 200 Hz and again at frequency of 10 kHz , 11 kHz .

$$X_c = \frac{1}{2\pi f C}$$

$$Z = R - jX_c$$

$$|Z| = \sqrt{R^2 + X_c^2}$$
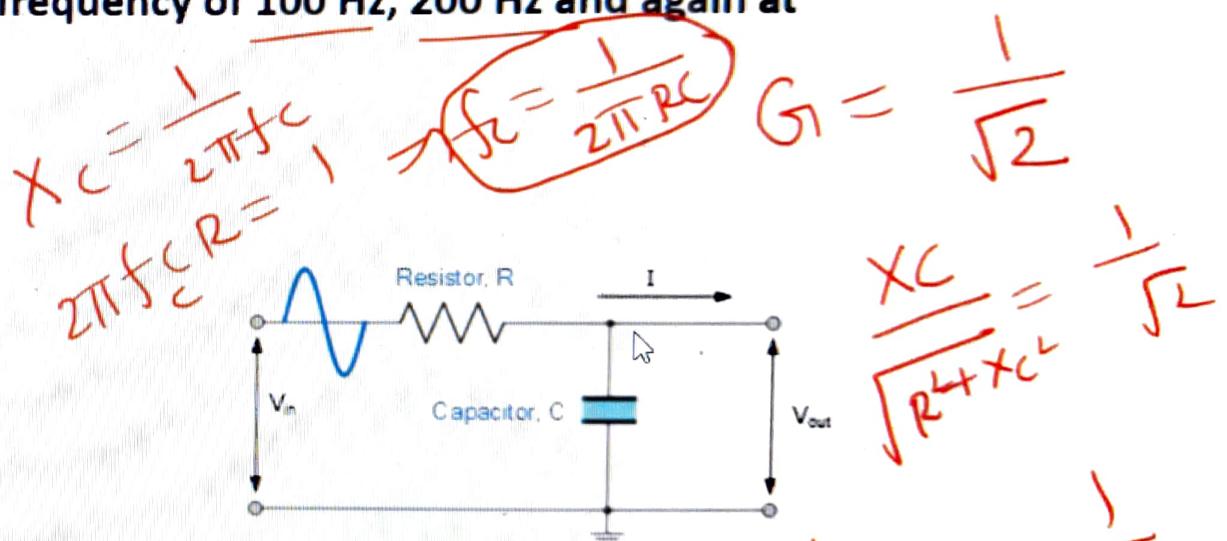
$$V_{\text{out}} = V_{\text{in}} \frac{X_c}{\sqrt{R^2 + X_c^2}} = V_{\text{in}} \frac{X_c}{Z}$$



$$\frac{R}{X_C} = 1$$

$$\frac{1}{(R/X_C)^2 + 1} = \frac{1}{2}$$