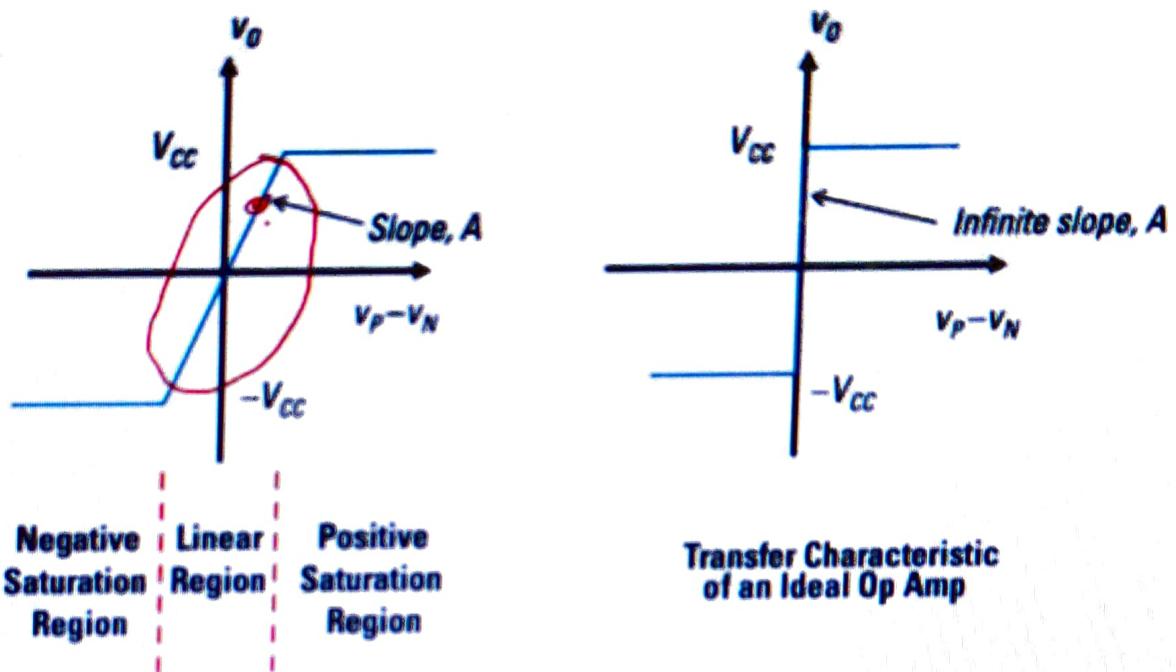


# Transfer characteristics of op-amp



Negative saturated region:  $v_o = -V_{cc}$

Linear active region:  $v_o = A_v(v_p - v_N)$

Positive saturated region:  $v_o = +V_{cc}$

Dr. E. Paul Brainerd

23



Raise hand



Turn on captions




# Transfer characteristics of op-amp

$$v_o > V_{CC}$$


$$if \quad v_o > V_{CC}$$

Saturation  $\approx -V_{CC}$

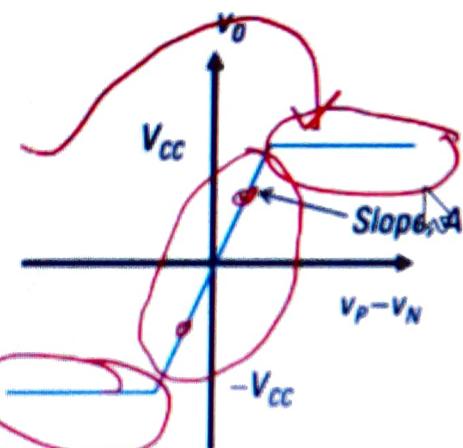Negative Saturation Region      Linear Region      Positive Saturation Region



$$+V_{CC}$$

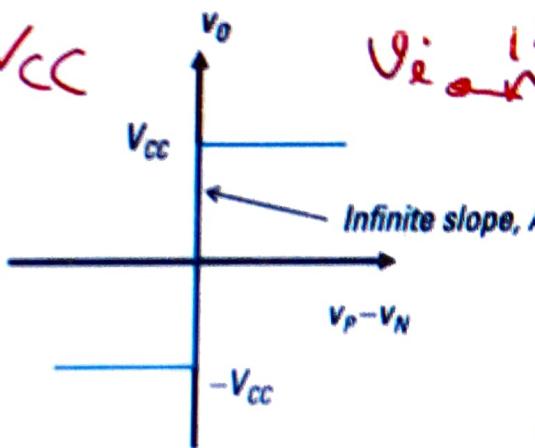


Transfer Characteristic  
of an Ideal Op Amp

$$\text{Negative saturated region: } v_o = -V_{CC}$$

$$\text{Linear active region: } v_o = A_v(v_p - v_N)$$

$$\text{Positive saturated region: } v_o = +V_{CC}$$

D. E. Paul, Braineering

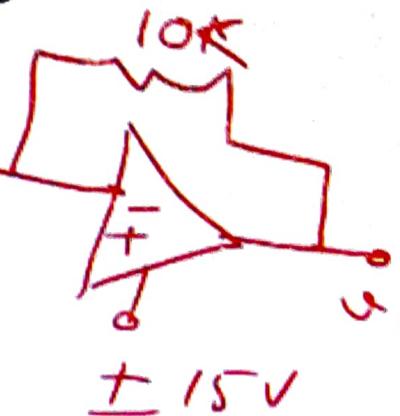

$$\text{gain} = 10$$

$$v_o = 10 v_i$$

$$if \quad v_i = 1 \text{ V}$$

$$v_o = -10 \text{ V} < V_{CC} + 15$$

$$v_i = 2 \text{ V}$$

$$v_o =$$

73



Raise hand




Turn on captions



*Saturation*
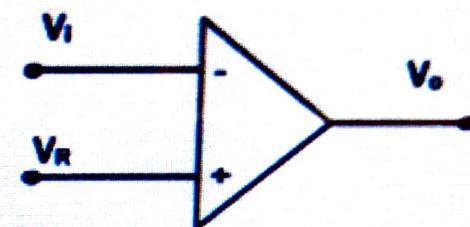
## Non-linear operation of op-amps

- Op-amp in open loop (no feedback)
  - Operates in non-linear fashion
- Open loop applications of op-amp
  - Comparators
  - Detectors
  - Converters etc.



Raise hand



Turn on captions




*Saturation*
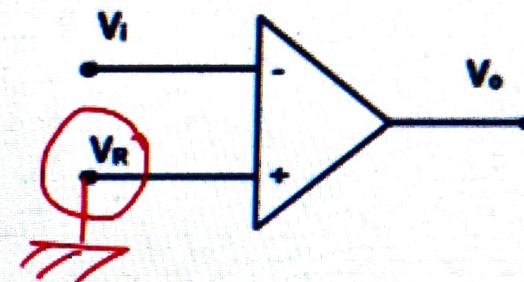
## Non-linear operation of op-amps

no feedback

- Op-amp in open loop (no feedback)
  - Operates in non-linear fashion
- Open loop applications of op-amp
  - Comparators
  - Detectors
  - Converters etc.



Compared     $V_R = 0$

$V_R = \pm 1$



Raise hand



Turn on captions

# Inverting Comparator

- Analog comparator has



- Two inputs

- A constant reference voltage  $V_R$  and other is a time varying signal  $v_i$

- One output  $v_o$

$$v_o = -V_{sat} \quad \text{if } v_i > V_R$$
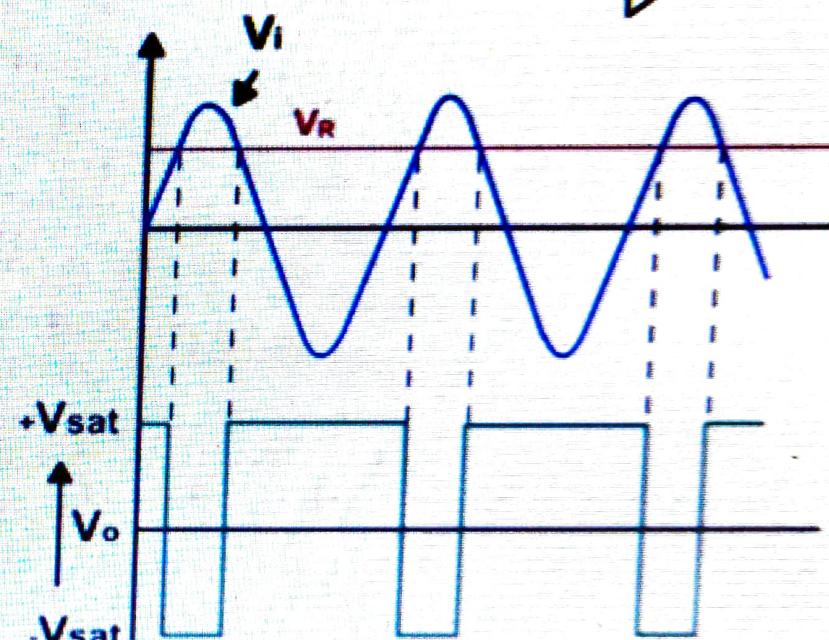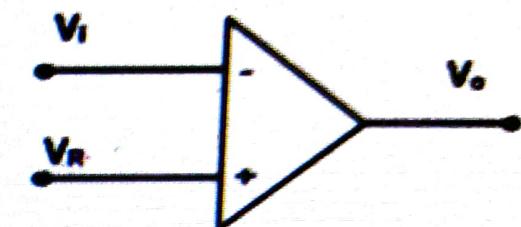
$$v_o = +V_{sat} \quad \text{if } v_i < V_R$$



$V_{sat}$   
 $14.8V$   
 $V_{CC} \leftarrow 15$

## Inverting Comparator

$$V^+ > V^- \Rightarrow V_o = +V_{sat}$$

- An analog comparator has



- Two inputs

- A constant reference voltage  $V_R$  and other is a time varying signal  $v_i$

- One output  $v_o$

$$v_o = -V_{sat} \quad \text{if } v_i > V_R$$
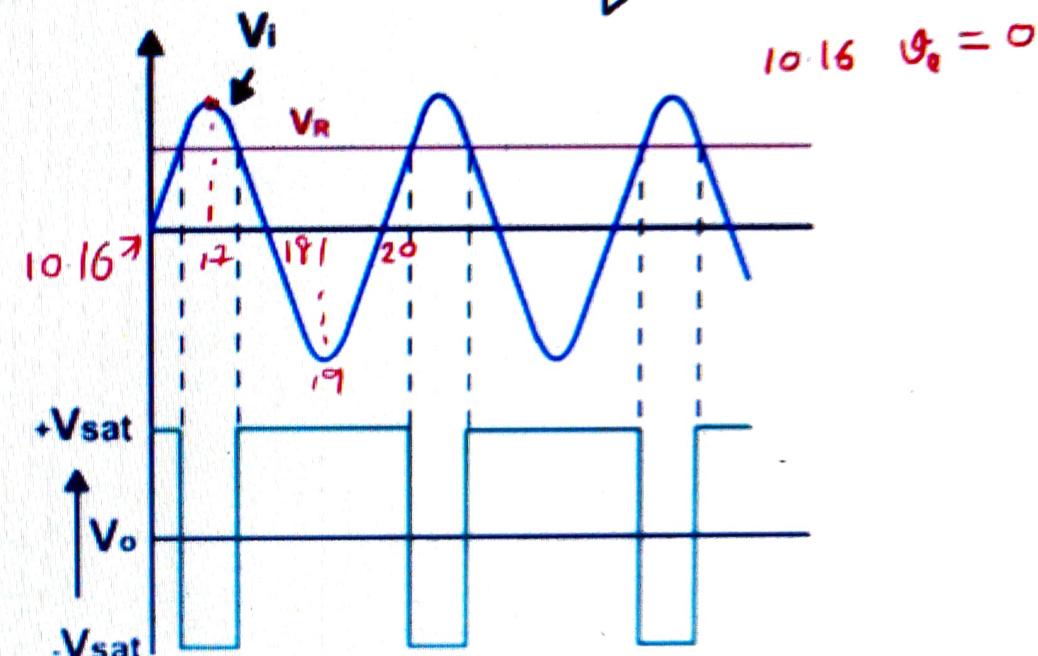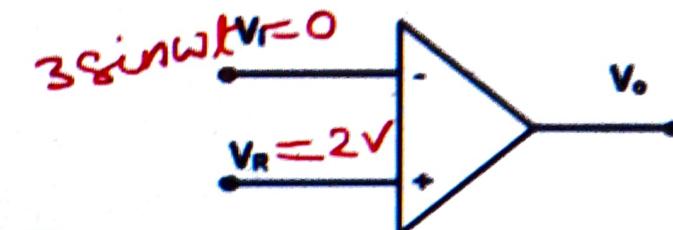
$$v_o = +V_{sat} \quad \text{if } v_i < V_R$$



Dr. E. Paul Bernath



Raise hand



Turn on captions



$V_{sat}$   $\underline{14} \underline{8V}$   $\underline{15}$   $V_{CC}$

$$V_i = V_R \leftarrow \text{theory}$$

## Inverting Comparator

$$V^+ > V^- \Rightarrow V_o = +V_{sat}$$

$$10.16 \rightarrow V_i = 0 \Rightarrow V^+ > V^- \Rightarrow V_o = +V_{sat}$$

$$10.17 \rightarrow V_i = 3V \Rightarrow V^- > V^+ \Rightarrow V_o = -V_{sat}$$



$$10.18 \rightarrow V_i = 0 \Rightarrow V^+ > V^- \Rightarrow V_o = +V_{sat}$$

$$10.19 \rightarrow V_i = -3 \Rightarrow 2 > -3 \Rightarrow V_o = +V_{sat}$$

$$10.20 \rightarrow V_i = 0 \Rightarrow 2 > 0 \Rightarrow V_o = +V_{sat}$$

$PW_{lb} \neq PW_{ub}$

$+VC = -Ve PW$

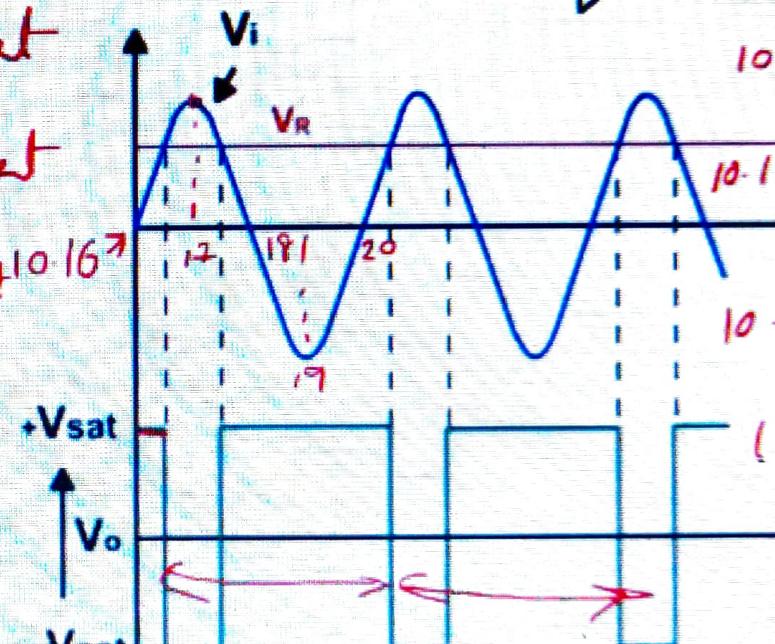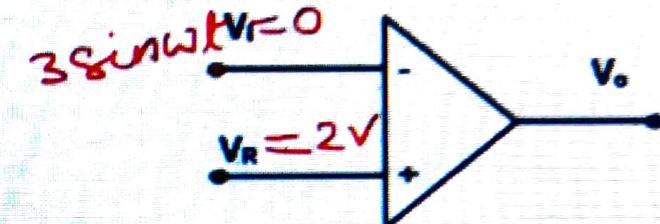

Raise hand



Turn on captions




$$\begin{array}{l} V_{sat} \\ \hline 14.8V \end{array} \quad \begin{array}{l} V_{CC} \\ \hline 15 \end{array}$$

~~$V_i = V_o$~~  ← theory ✓

## Inverting Comparator

$$V^+ > V^- \Rightarrow V_o = +V_{sat}$$

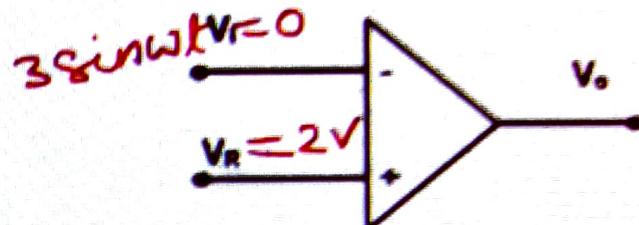

$$10.16 \rightarrow V_i = 0 \Rightarrow V^+ > V^- \Rightarrow V_o = +V_{sat}$$

$$10.17 \rightarrow V_i = 3V \Rightarrow V^- > V^+ \Rightarrow V_o = -V_{sat}$$


$$10.18 \rightarrow V_i = 0 \Rightarrow V^+ > V^- \Rightarrow V_o = +V_{sat}$$

$$10.19 \rightarrow V_i = -3 \Rightarrow 2 > -3 \Rightarrow V_o = +V_{sat}$$

$$10.20 \rightarrow V_i = 0 \Rightarrow 2 > 0 \Rightarrow V_o = +V_{sat}$$

~~HW~~  $\#$  ~~HW~~

$$+V_C = -V_{sat}$$

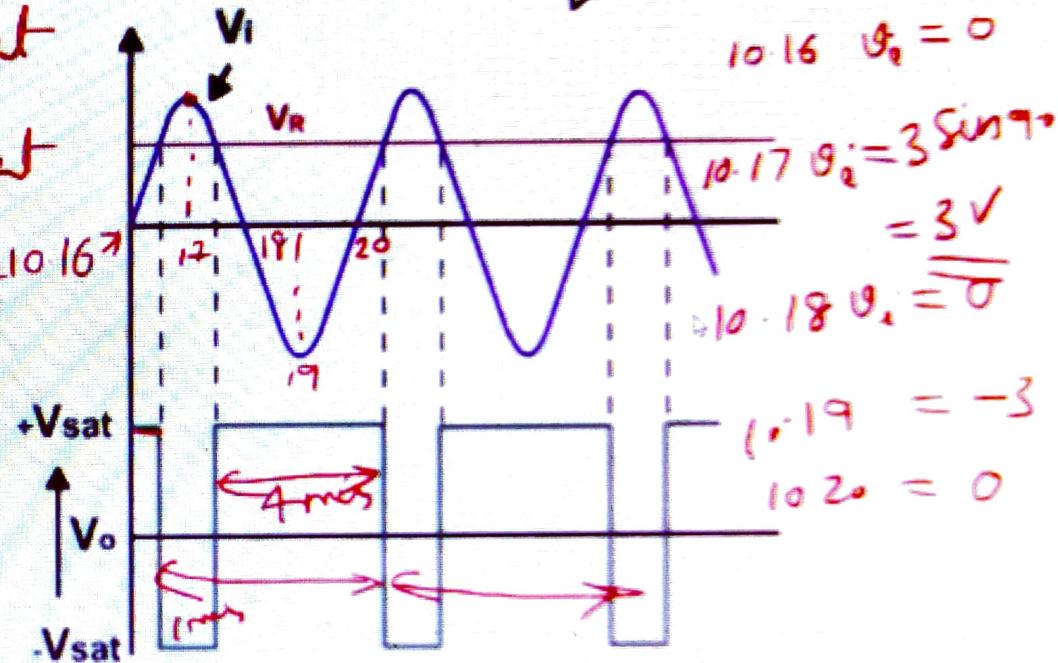

Dr. F. Paul Brainboard




Raise hand



Turn on captions



# Zero crossing detector

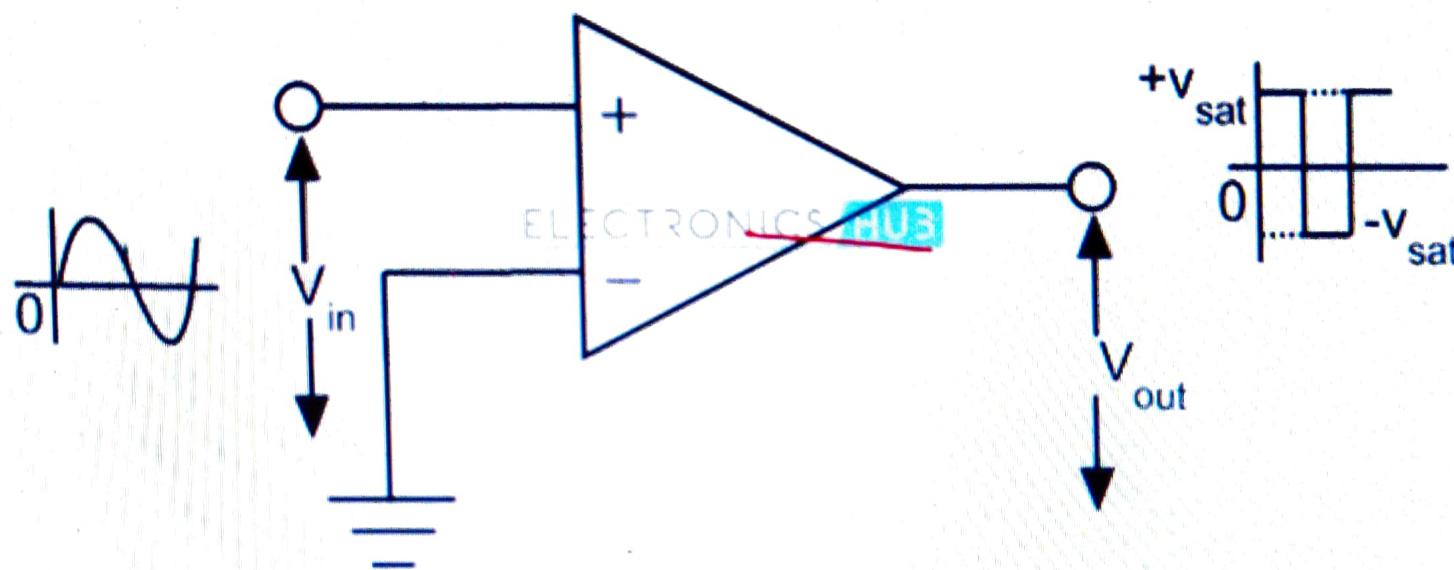

Dr. E. Paul Braneard

60




Raise hand



Turn on captions



# Three level comparator with LED

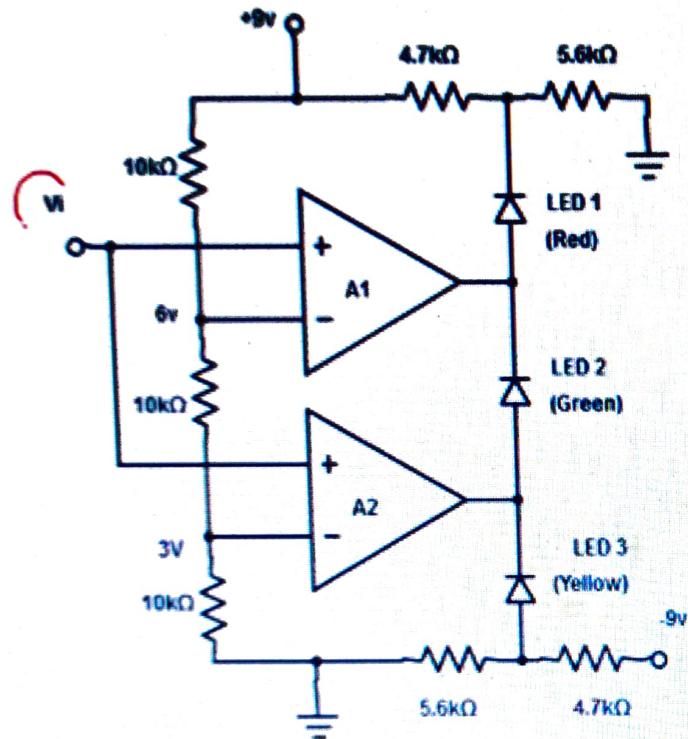

Input ( $V$ )	LED 3 (Red)	LED 2 (Green)	LED 1 (Yellow)
$< 3$			
$3 < v_i < 6$			
$> 6$			

Dr. E. Ravat Brahmeur

53




Raise hand



Turn on captions



# Three level comparator with LED

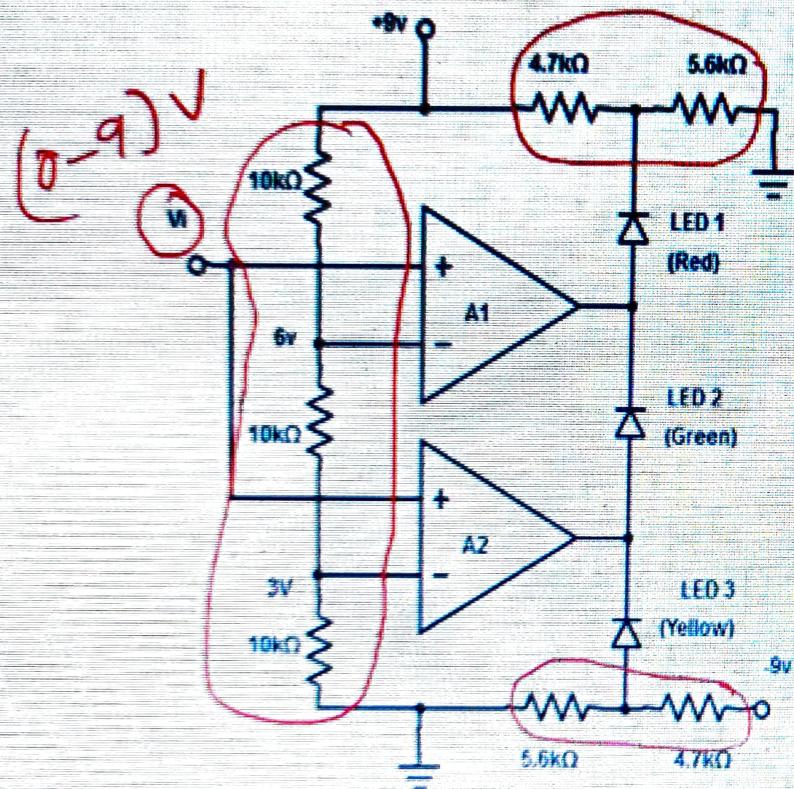

Input (V)	LED 3	LED 2	LED 1
$< 3$			
$3 < v_i < 6$			
$> 6$			

Dr. K. Srinivas Reddy

87



Raise hand



Turn on caption




$$V_{R1} = \frac{20}{30} \times 9 = 6V$$

$$V_{R2} = 3V$$

$\sum R_1 = V_{R1}$   
 $\sum R_2 = V_{R2}$   
 $\sum R_3 = V_R$
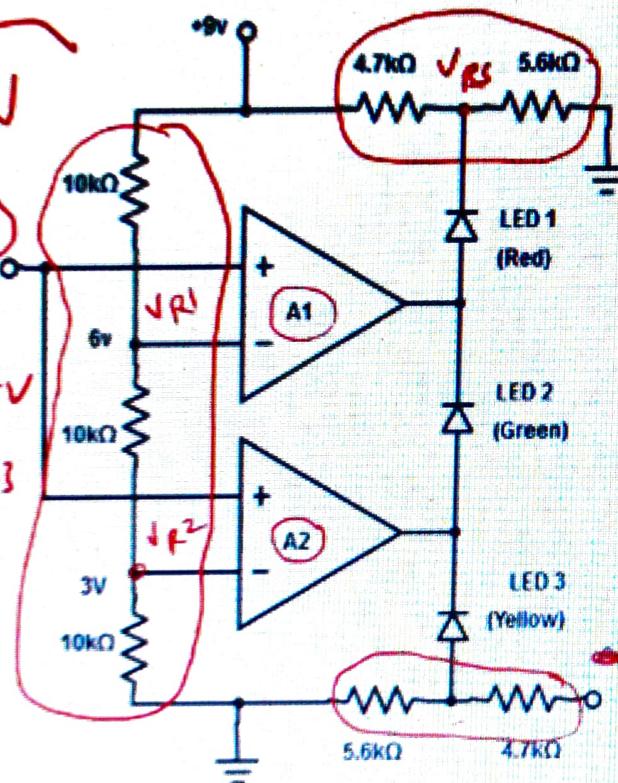
$$V_R = \frac{R_2 + R_3}{R_1 + R_2 + R_3} 9V$$



# Three level comparator with LED

Input (V)	LED 3	LED 2	LED 1
$< 3$			
$3 < v_i < 6$			
$> 6$			

Q1. Place Boundary




Raise hand



Turn on captions

$$V_{R1} = \frac{20}{30} \times 9 = 6V$$

## Three level comparator with LED

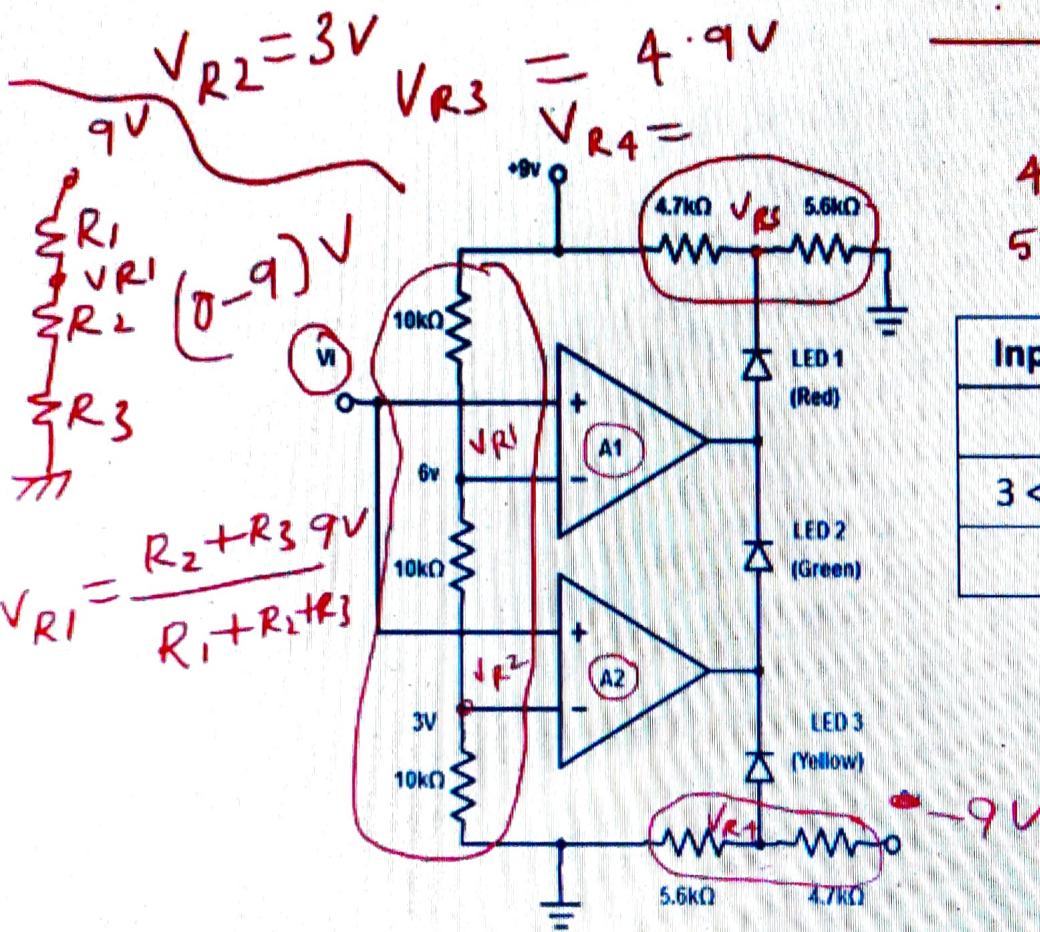

$$V_{R3} = \frac{4.7}{4.7 + 5.6} \times 9V = \frac{4.7}{10.3} \times 9V = 4.39V$$

Input (V)	LED 3	LED 2	LED 1
$< 3$			
$3 < v_i < 6$			
$> 6$			



Raise hand




Turn on captions



$$V_{R1} = \frac{20}{30} \times 9 = 6V$$

# Three level comparator with LED

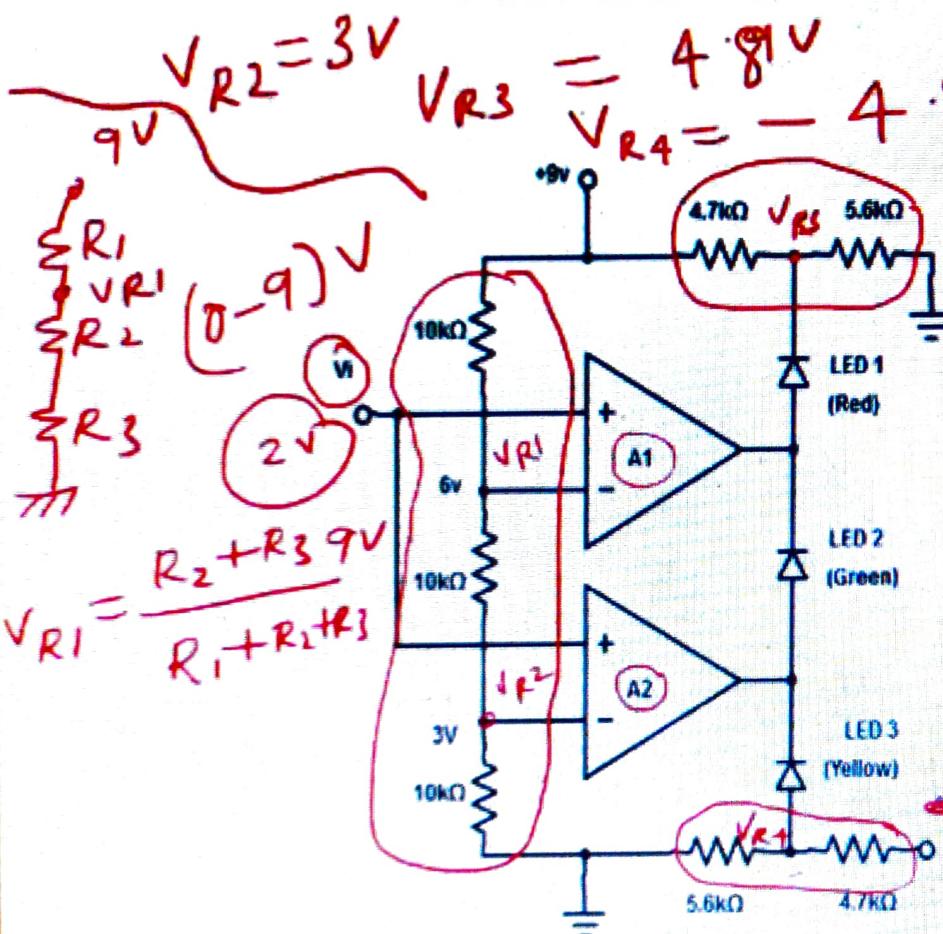

$$V_{R3} = \frac{5.6}{4.7 + 5.6} \times 9 = 4.89V$$

Input (V)	LED 3	LED 2	LED 1
$< 3$			
$3 < v_i < 6$			
$> 6$			

$$V_{R4} = \frac{5.6}{4.7 + 5.6} \times -9 = -4.89V$$



Raise hand




Turn on captions



$$V_{R1} = \frac{20}{30} \times 9 = 6V$$

# Three level comparator with LED

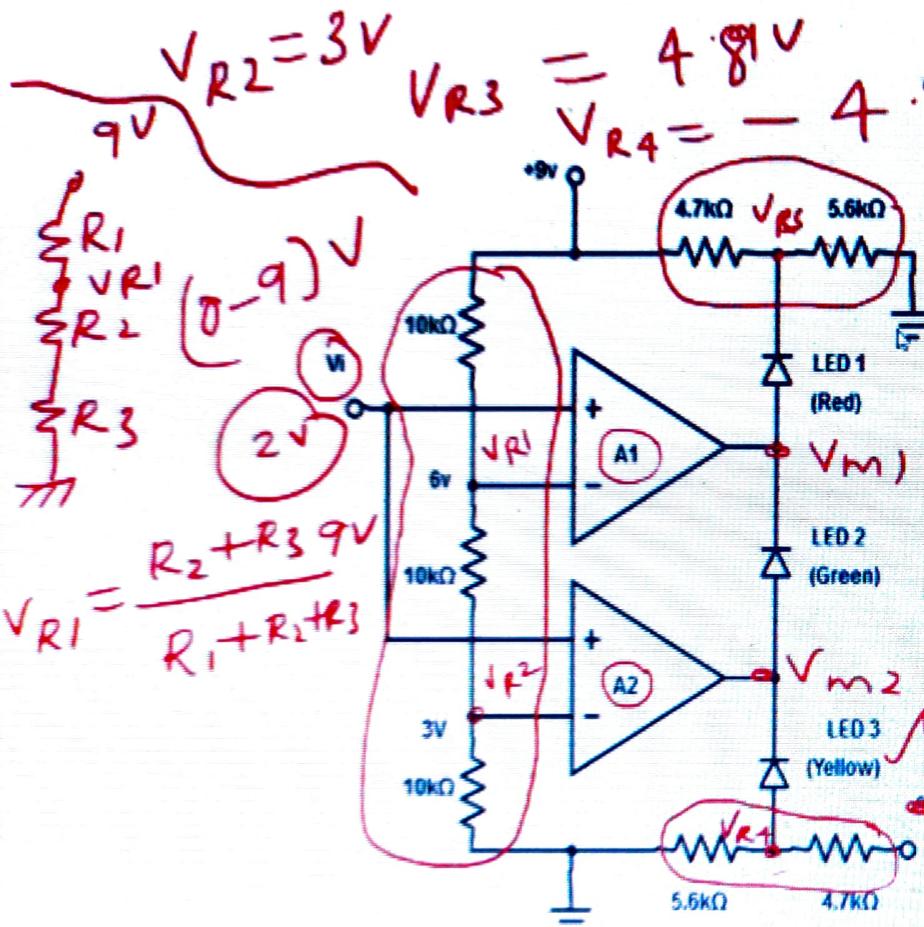

$$\frac{9}{4.7+5.6} \times 9 = 4.89V$$

Input (V)	LED 3	LED 2	LED 1
$< 3$			
$3 < v_i < 6$			
$> 6$			

$$V_{R4} = \frac{5.6 \times -9}{4.7 + 5.6} = -4.89V$$

Dr. E. Phal Bhamare, M.Tech.

52



Raise hand



Turn on captions

